

4. Logic Gates.

(Marks:-17)

Q.1 Logic Gates:-

Ans.

Gate is an electronic circuit in which only one input & two or more than output.

➤ There are three basic types of logic gates:-

1. AND Gate.
2. OR Gate.
3. NOT Gate. [Bubble/ Inverter Gate]

Logic Decision:-

Inter connection of gate to perform variety of logic decision operation is called logic decision.


Truth Table:-

A table which list all the possible communication of Input variable & corresponding output is called truth table.

1. AND Gate :-

AND Gate is logical gate in which two or more input & only one output.

Block Diagram of AND Gate:-

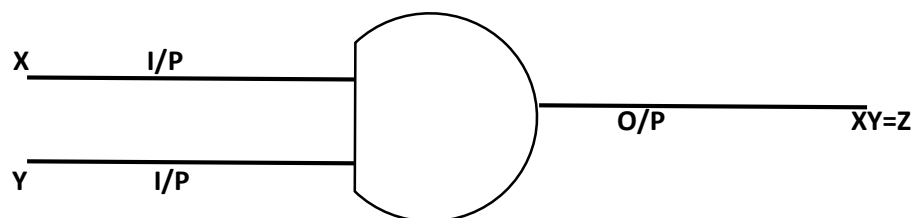

Truth table of AND Gate:-

Input		Output
X	Y	Z=XY
0	0	0(low)
0	1	0
1	0	0
1	1	1(High)


Explain:-

If both input are low then output low, if both input are high then output high otherwise output is low.

2. OR Gate:-

OR Gate is two or more than input & only one output.

Block Diagram of OR Gate:-

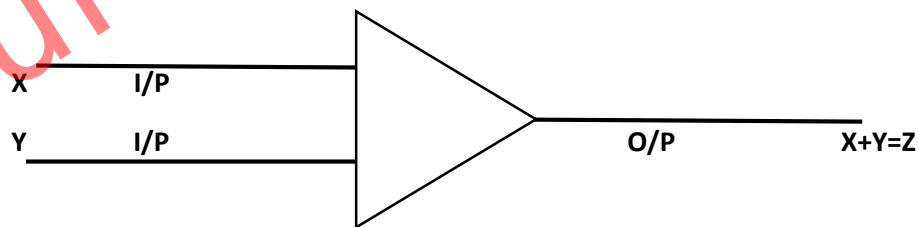

Truth table of OR Gate:-

Input		Output
X	Y	$Z=X+Y$
0	0	0(Low)
0	1	1
1	0	1
1	1	1(High)


Explain:-

If both input are low than output will be low otherwise output will be high. If any input high than output will be high.

3. NOT Gate [Bubble/ Inverter Gate]:-

Not Gate is inverter gate. It has only one input & only one output. It contain bubble to inverter.

Block diagram of NOT Gate:-

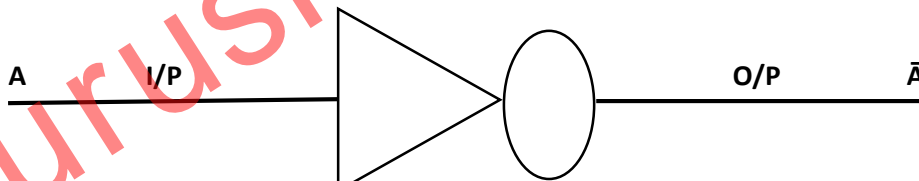

Truth table of NOT Gate:-

Input	Output
A	\bar{A}
0	1
1	0

Explain:-

If input is low than output is high & if input is high than output is low.

Q.2 Universal Gate:-

Ans.

➤ There are two types of universal gate.

1. NAND [AND + NOT]


2. NOR [OR + NOT]

NAND & NOR perform all three basic logic [AND, OR, NOT] that's way is called universal gate.

1. NAND [AND + NOT]:-

NAND Gate is universal gate in which two or more than two input & only one output.

Block diagram of NAND Gate:-

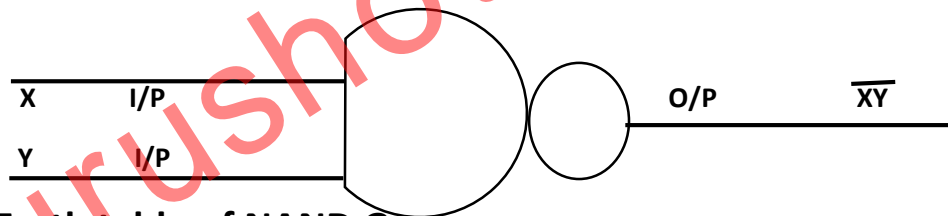

Truth table of NAND Gate:-

Input		Output	
X	Y	XY	\overline{XY}
0	0	0	1
0	1	0	1
1	0	0	1
1	1	1	0

Explain:-


If both input are high then output will be low. Otherwise output will be high.

NAND Gate is communication is AND & NOT gate.

2. NOR[OR+NOT] :-

NOR is universal gate in which two or more than two input & only one output.

Block diagram of NOR Gate:-

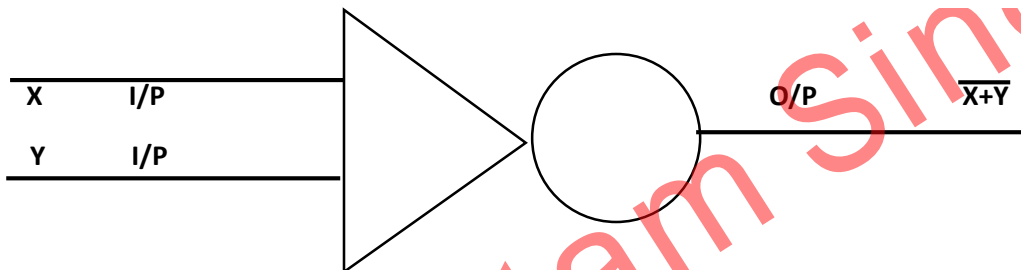

Truth table of NOR Gate:-

Input		Output	
X	Y	X+Y	$\overline{X+Y}$
0	0	0	1
0	1	1	0
1	0	1	0
1	1	1	0

Explain:-


If both input are low than output is high, otherwise input is high than output will be low.

NOR Gate is communication of OR+NOT Gate.

Q.3 Exclusive- OR-Gate [ex-OR]... [$\bar{A}B + A\bar{B}$] or [$A (+) B$].

Ans.

Block Diagram of Exclusive OR Gate:-

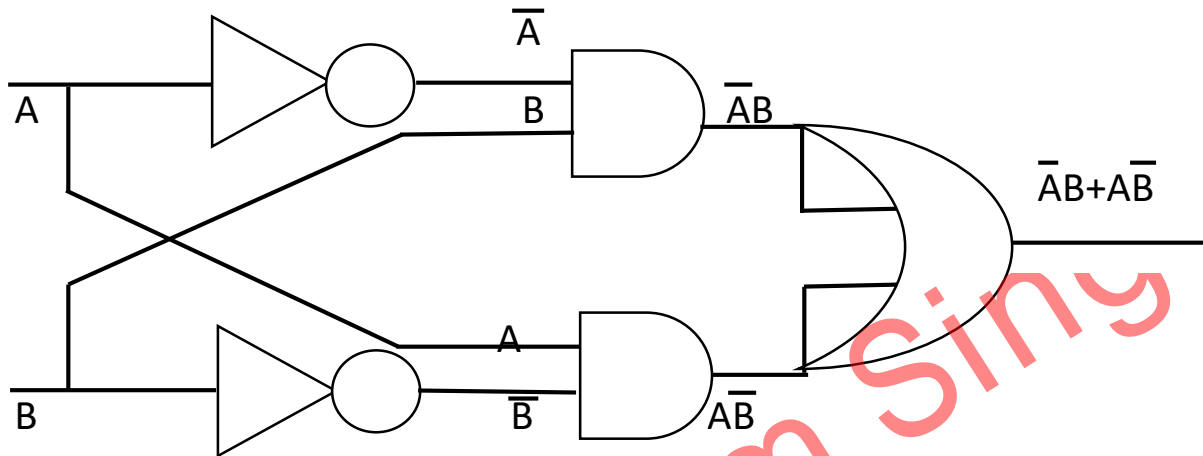


Truth table of Exclusive OR Gate:-

Input				Output		
A	B	\bar{A}	\bar{B}	$\bar{A}B$	$A\bar{B}$	$\bar{A}B + A\bar{B}$
0	0	1	1	0	0	0
0	1	1	0	1	0	1
1	0	0	1	0	1	1
1	1	0	0	0	0	0

Q.4 Exclusive- NOR-Gate [ex-NOR]... $\overline{\overline{A}B + A\overline{B}}$.

Ans.

Block Diagram of Exclusive NOR Gate:-

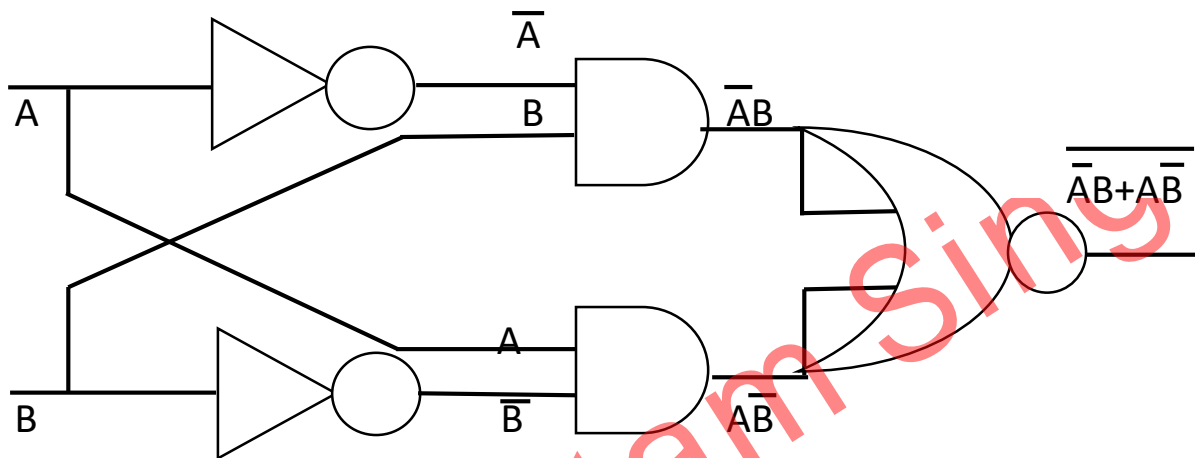

Truth table of Exclusive NOR Gate:-


Input				Output			
A	B	\overline{A}	\overline{B}	$\overline{A}B$	$A\overline{B}$	$\overline{A}B + A\overline{B}$	$\overline{\overline{A}B + A\overline{B}}$
0	0	1	1	0	0	0	1
0	1	1	0	1	0	1	0
1	0	0	1	0	1	1	0
1	1	0	0	0	0	0	1

Q.5 Combinational Circuit

Ans.

In combinational circuit output is depend on only present input.

Block diagram of combinational:-

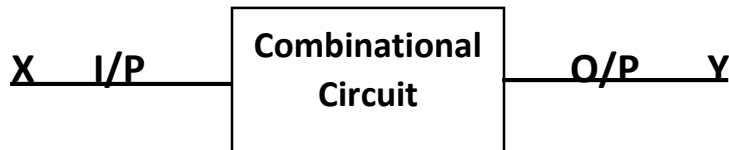

➤ There are two types of combinational circuit.

1. Adder

I. Half adder (0+0)

II. Full adder(0+0+0)

2. Subtraction

I. Half subtraction(0-0)

II. Full subtraction (0-0-0)

1. Adder:-

In combinational circuit perform addition of bit is called adder.

- There are two types of adder:-


I. Half adder (0+0)

II. Full adder(0+0+0)

I. Half adder (0+0) :-

In communicational circuit which can perform the addition of two bit is called half adder.

Block diagram of Half adder:-

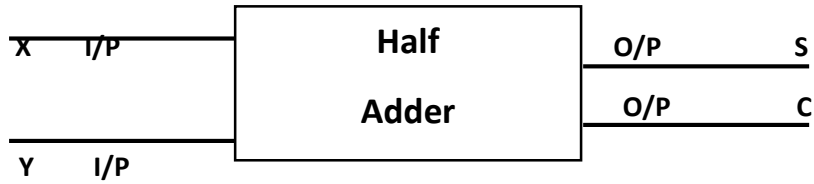


Truth table of Half adder:-

Input		Output	
X	Y	S	C
0	0	0	0
0	1	1	0
1	0	1	0
1	1	0	1


Logic of Half adder of Sum:-

$$[\bar{X}Y + X\bar{Y}]$$

Circuit of Half adder of Sum: -

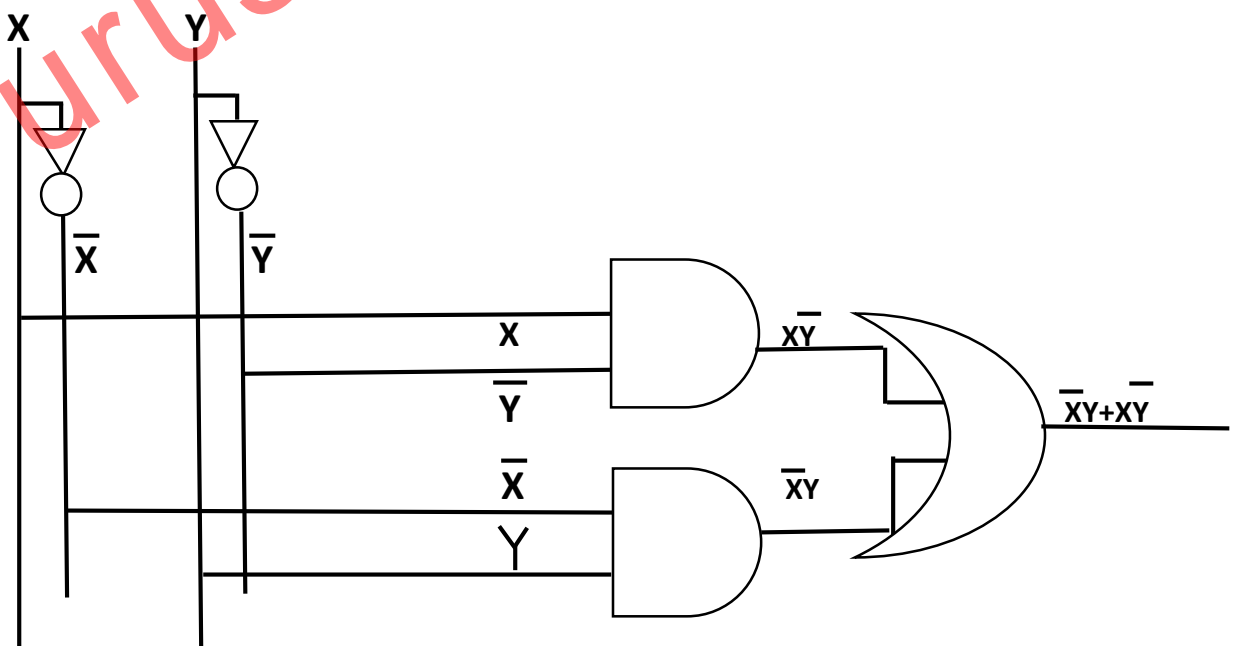

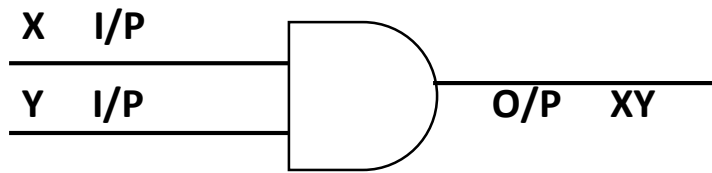
Circuit of Half adder of carry: - [logic: - XY]



II. Full adder(0+0+0) :-

In communication can which three bit addition is called full adder.

Block diagram of Full adder:-

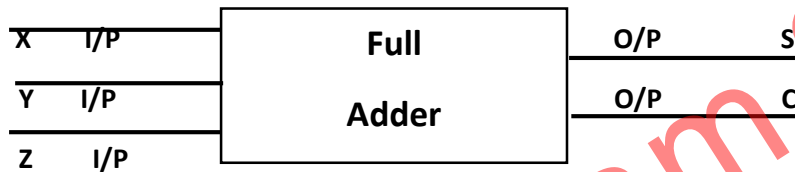

Truth table of Full adder:-

Input			Output	
X	Y	Z	S	C
0	0	0	0	0
0	0	1	1	0
0	1	0	1	0
0	1	1	0	1
1	0	0	1	0
1	0	1	0	1
1	1	0	0	1
1	1	1	1	1

Logic of Full adder of sum:-

$$= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$= \bar{X} (\bar{Y} Z + Y \bar{Z}) + X (\bar{Y} \bar{Z} + Y Z)$$

$$= \bar{X} (Y (+) Z) + X (\overline{Y (+) Z})$$


$$= (\bar{Y} (+) \bar{Z}) = K_{\text{Carry}}$$

$$= XK + XK$$

$$= X (+) K$$

$$= X (+) Y (+) Z$$

Circuit of Full adder of sum:-

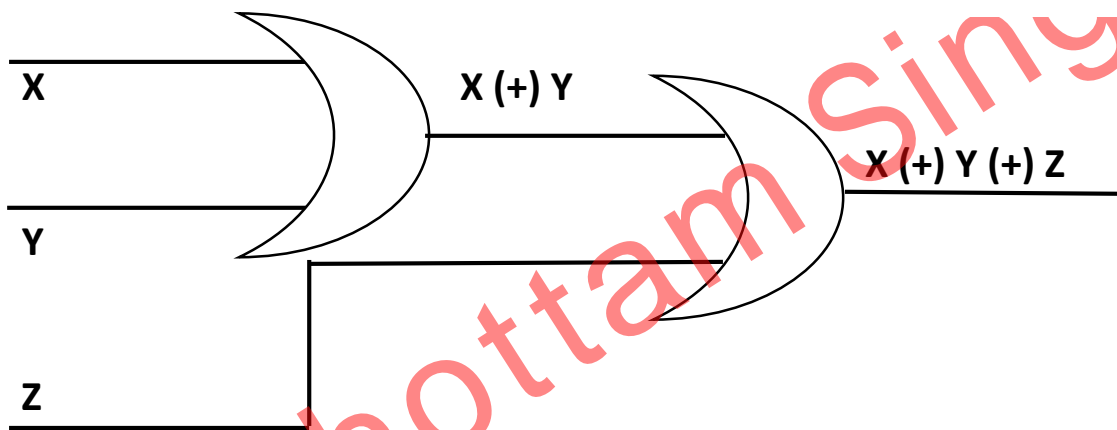

Logic of Full adder of carry:-


$$= \bar{X} Y Z + X \bar{Y} Z + X Y \bar{Z} + X Y Z$$

$$= Z (\bar{X} Y + X \bar{Y}) + X Y (\bar{Z} + Z)$$

$$= Z (X (+) Y) + X Y (1)$$

$$= ZX + ZY + XY$$

Circuit of Full adder of carry:-

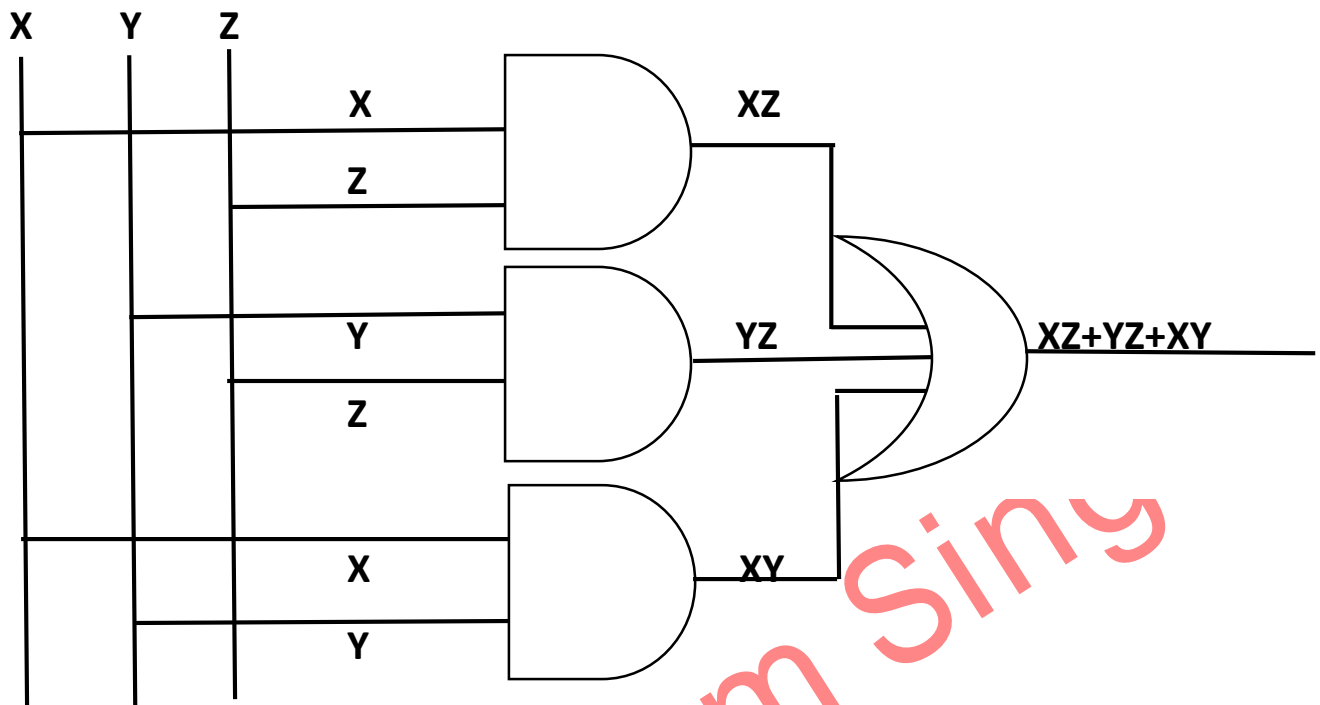

2. Subtraction:-


There are two types of subtraction:-

- I. Half subtraction (0-0)
- II. Full subtraction (0-0-0)

I. Half subtraction(0-0):-

In communicational circuit which can perform difference between two bit.

Block diagram of half subtraction:-

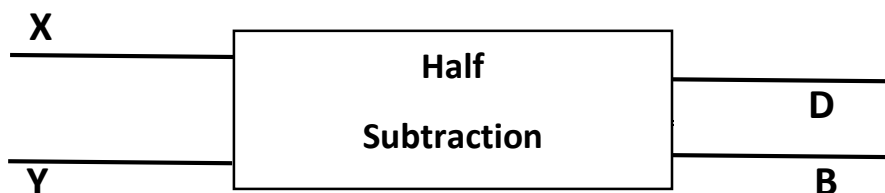

Truth table of half subtraction:-


Input		Output	
X	Y	D	B
0	0	0	0
0	1	1	1
1	0	1	0
1	1	0	0

Logic of half subtraction of Difference:-

$$= \bar{X}Y + X\bar{Y}$$

$$= X (+) Y$$

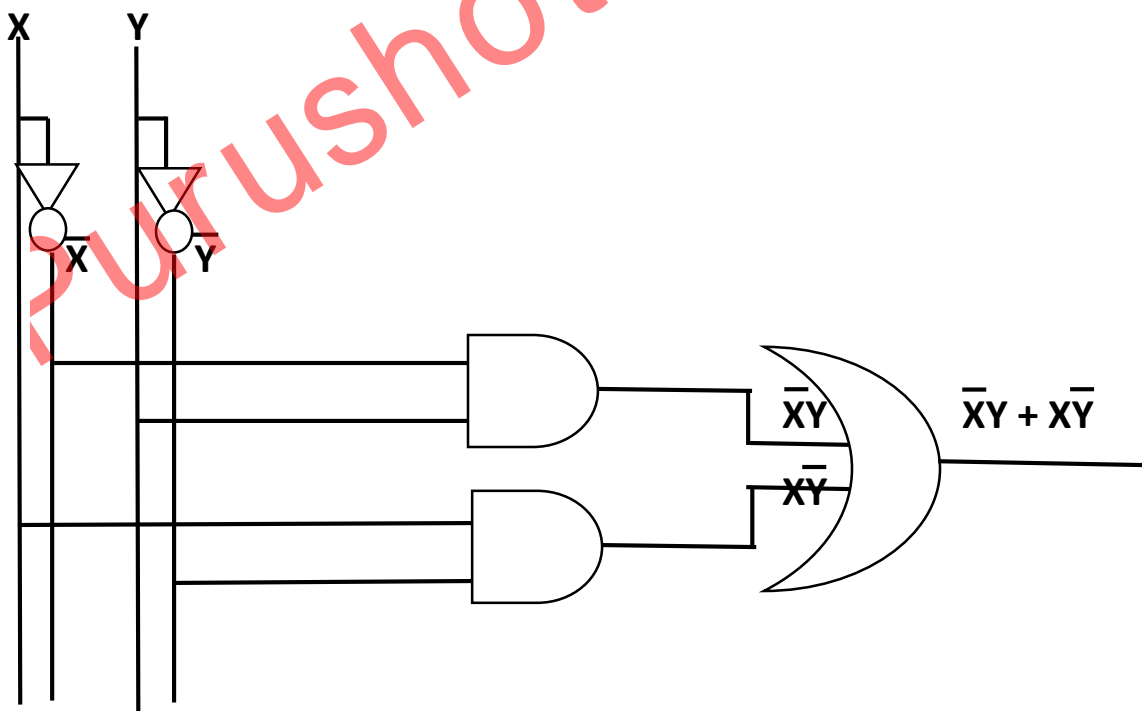
Circuit of half subtraction of difference:-



Logic of half subtraction of borrow:-

$$= \bar{X}Y$$


Circuit of half subtraction of borrow:-

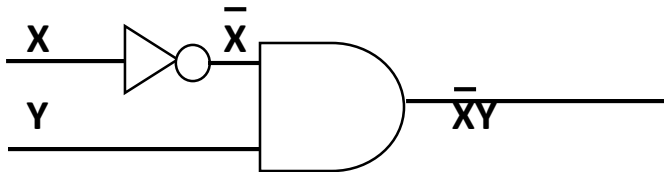

II. Full subtraction (0-0-0):-

In communicational circuit which can perform different between 3 bits is called full subtraction.

Block diagram of full subtraction:-

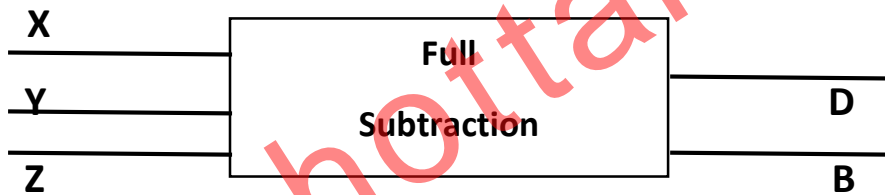

Truth table of full subtraction:-

Input			Output	
X	Y	Z	D	B
0	0	0	0	0
0	0	1	1	1
0	1	0	1	1
0	1	1	0	1
1	0	0	1	0
1	0	1	0	0
1	1	0	0	0
1	1	1	1	1

Logic of full subtraction of different:-

$$= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$= \bar{X} (Y (+) Z) + X (\overline{Y (+) Z})$$

$$= Y (+) Z = K \text{ થારતી}$$


$$= \bar{X}(K) + X(\bar{K})$$

$$= X (+) K$$

$$= X (+) Y (+) Z$$

$$K = Y (+) Z \text{ મૂકતી.}$$

Circuit of subtraction of difference:-

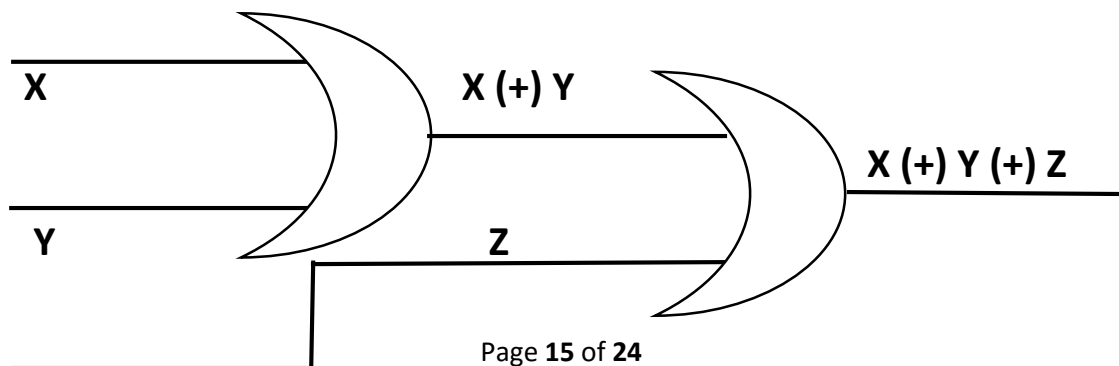

Logic of full subtraction of borrow:-


$$= \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + \bar{X}YZ + XYZ$$

$$= \bar{X} (\bar{Y}Z + Y\bar{Z}) + YZ (\bar{X} + X)$$

$$= \bar{X} (Y \oplus Z) + YZ (1)$$

$$= \bar{X}Y + \bar{X}Z + YZ$$

Circuit of full subtraction of borrow:-

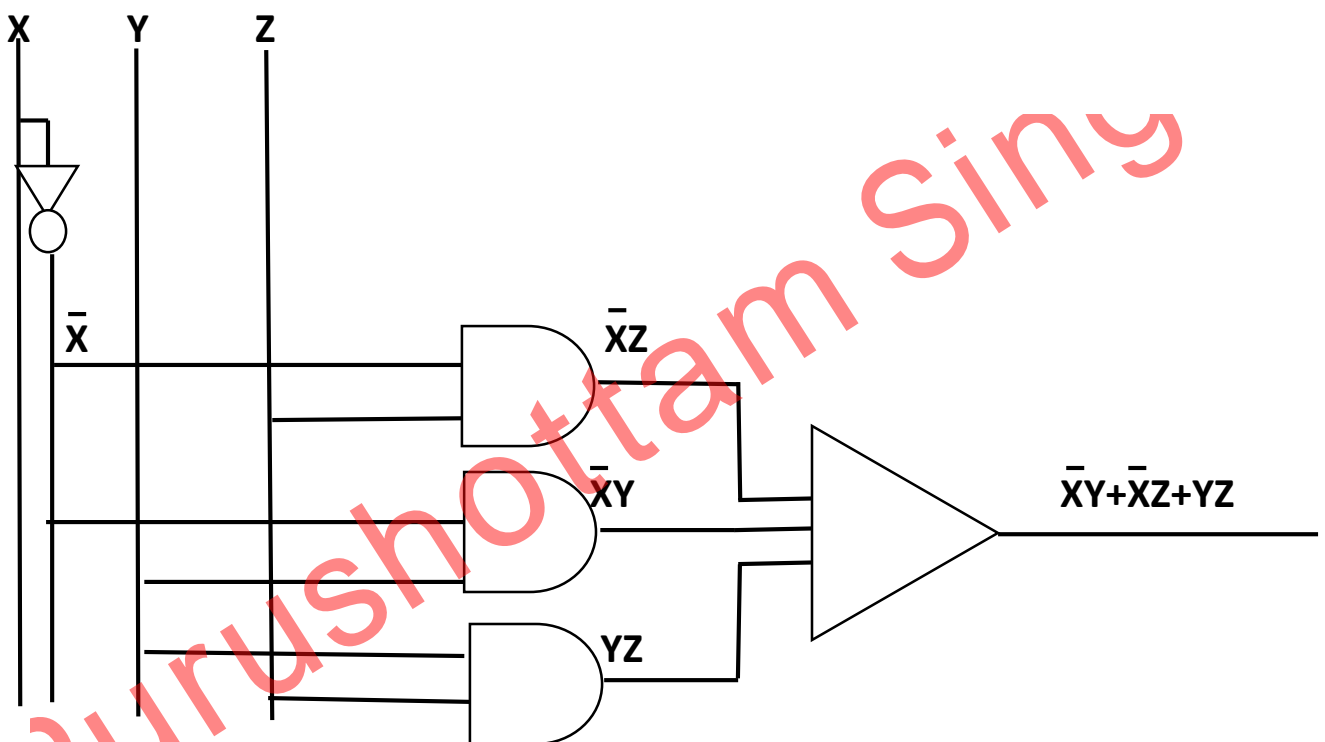

Q.6 Decoder:-

Ans.

Decoder is combinational that convert binary Information from n input line 2^n output line.

Block diagram of Decoder:-




➤ There are two types of decoder:-

1. **(2*4) Decoder or 2*4 line Decoder.**
2. **(3*8) Decoder or 3*8 line Decoder.**

1. (2*4) Decoder or 2*4 line Decoder:-

A Decoder is having two input line & $2^n = 2^2 = 2*2 = 4$ decoder is called 2*4 decoder.

Block diagram of 2*4 Decoder:-

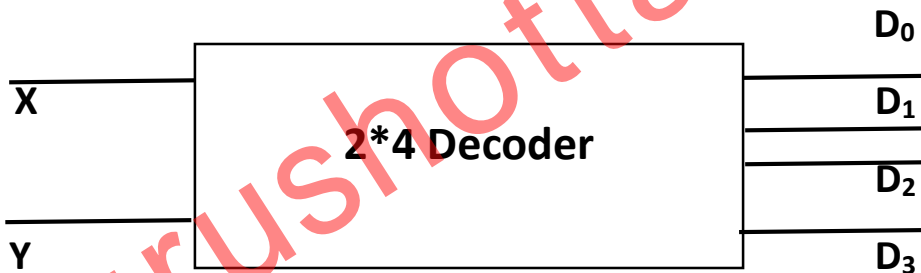

Truth table of 2*4 Decoder:-


Input		Output			
X	Y	D ₀	D ₁	D ₂	D ₃
0	0	1	0	0	0
0	1	0	1	0	0
1	0	0	0	1	0
1	1	0	0	0	1

Logic of 2*4 Decoder:-

$$D_0 = \bar{X}\bar{Y} \quad D_2 = X\bar{Y}$$

$$D_1 = \bar{X}Y \quad D_3 = XY$$


Circuit of 2*4 Decoder:-

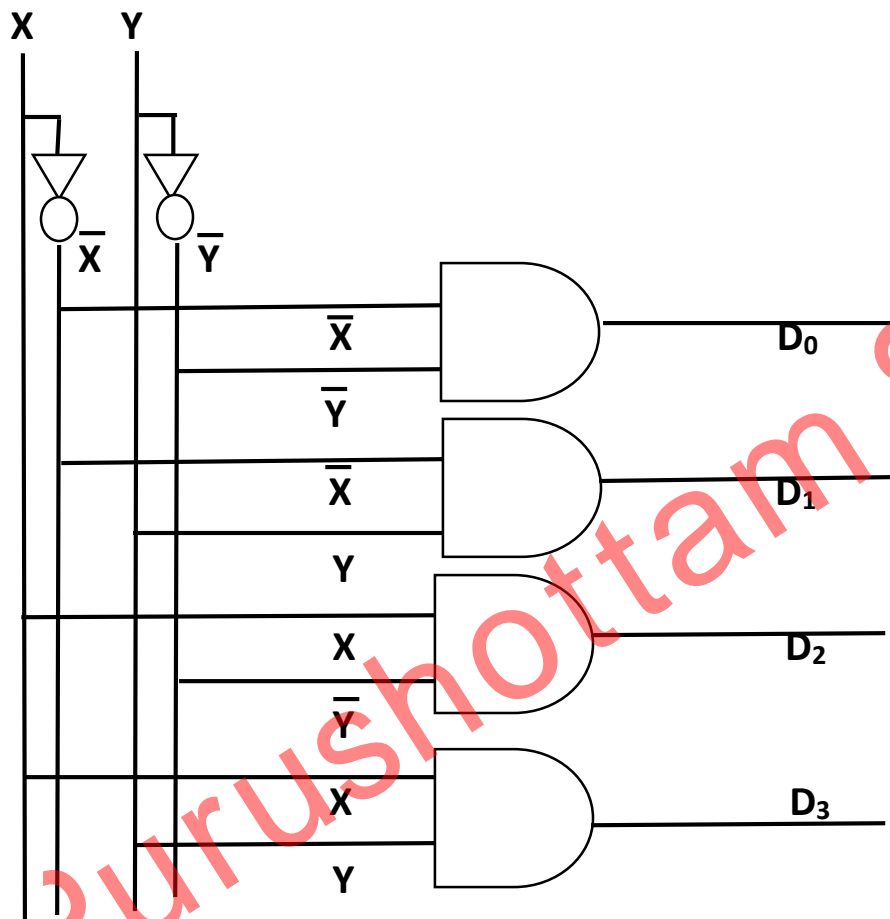

2. 3*8 Decoder or 3*8 line Decoder:-

A decoder having three input line $2^n = 2^3 = 2 * 2 * 2 = 8$ output line is called 3*8 decoder.

Block diagram of 3*8 line Decoder:-

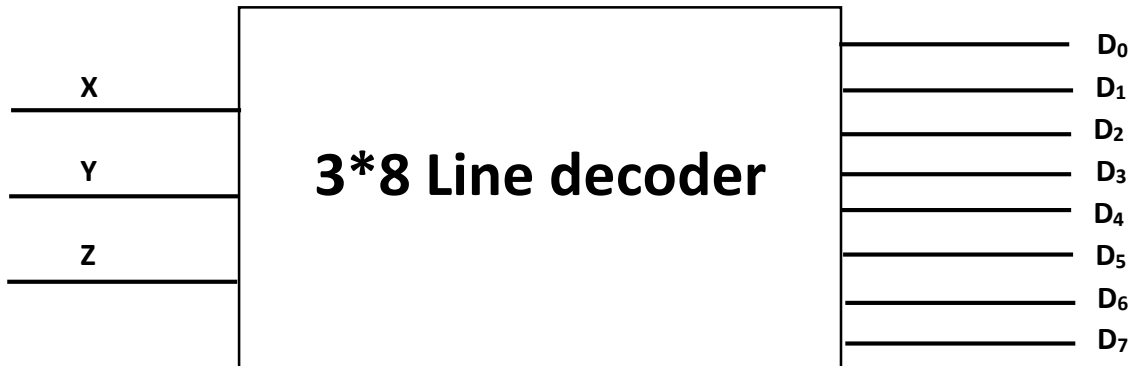

Truth table of 3*8 line Decoder:-


Input			Output (Octal)							
X	Y	Z	D ₀	D ₁	D ₂	D ₃	D ₄	D ₅	D ₆	D ₇
0	0	0	1	0	0	0	0	0	0	0
0	0	1	0	1	0	0	0	0	0	0
0	1	0	0	0	1	0	0	0	0	0
0	1	1	0	0	0	1	0	0	0	0
1	0	0	0	0	0	0	1	0	0	0
1	0	1	0	0	0	0	0	1	0	0
1	1	0	0	0	0	0	0	0	1	0
1	1	1	0	0	0	0	0	0	0	1

Logic of 3*8 line Decoder:-

$$D_0 = \bar{X} \bar{Y} \bar{Z} \quad D_3 = \bar{X} Y Z \quad D_6 = X Y \bar{Z}$$

$$D_1 = \bar{X} \bar{Y} Z \quad D_4 = X \bar{Y} \bar{Z} \quad D_7 = X Y Z$$
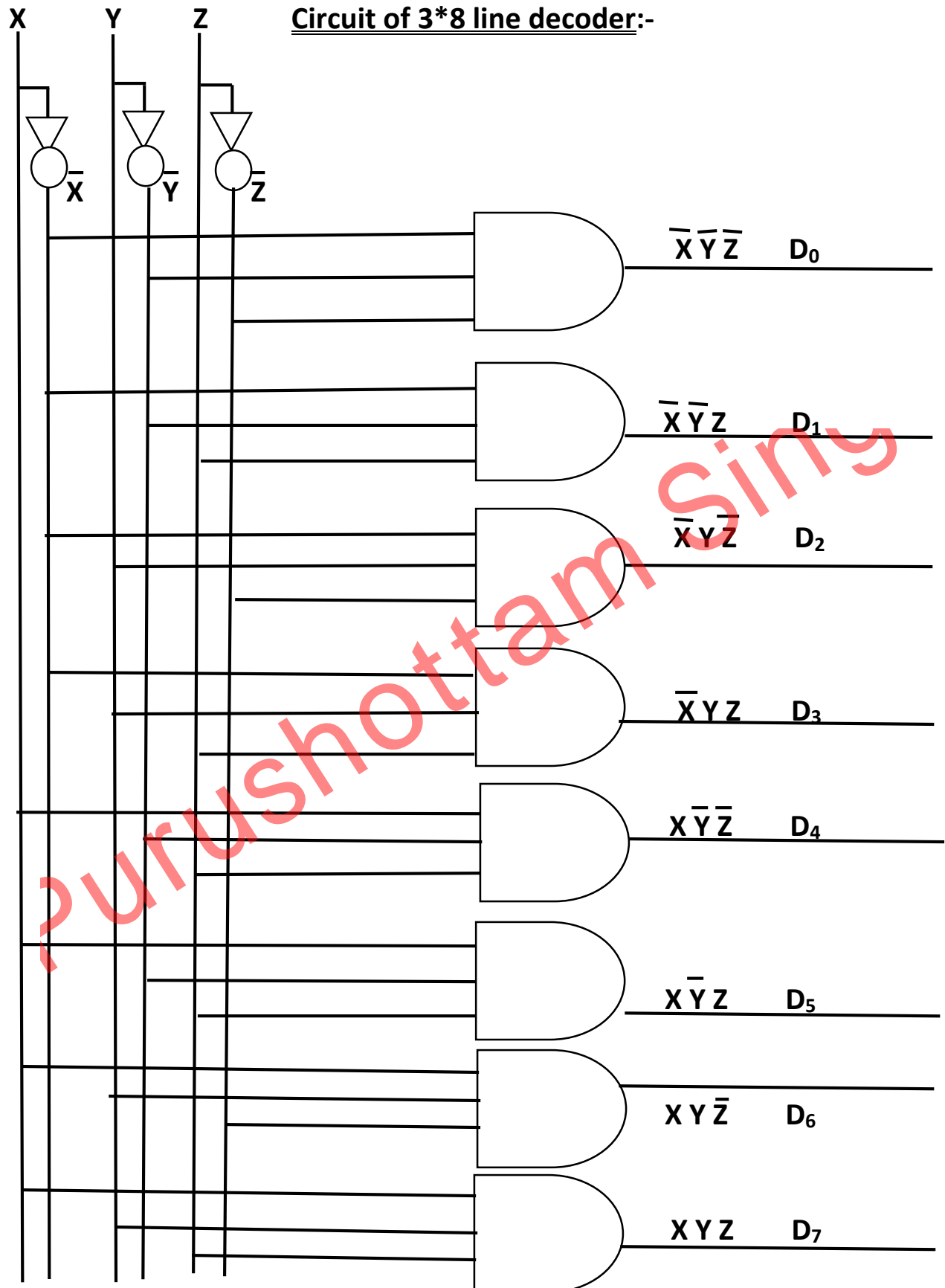
$$D_2 = \bar{X} Y \bar{Z} \quad D_5 = X \bar{Y} Z$$




Q.7 Encoder:-

Ans.

Encoder is digital circuit that product operation from decoder. Encoder has 2^n input & n output line.

Block diagram of encoder:-

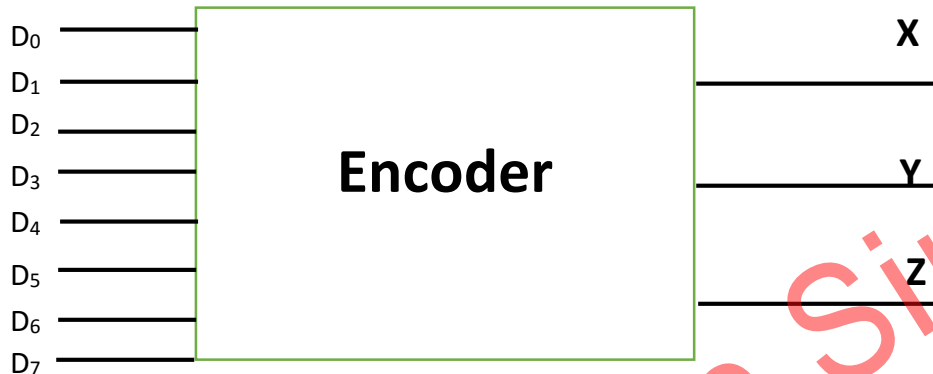

Explain:-

Octal to binary encoder consist of 8 input & 3 output which generate binary run.

Truth table of encoder:-

Input	Output		
Octal	X	Y	Z
D ₀	0	0	0
D ₁	0	0	1
D ₂	0	1	0
D ₃	0	1	1
D ₄	1	0	0
D ₅	1	0	1
D ₆	1	1	0
D ₇	1	1	1


Logic of encoder:-

$$X = D_4 + D_5 + D_6 + D_7$$

$$Y = D_2 + D_3 + D_6 + D_7$$

$$Z = D_1 + D_3 + D_5 + D_7$$

Circuit of encoder:-

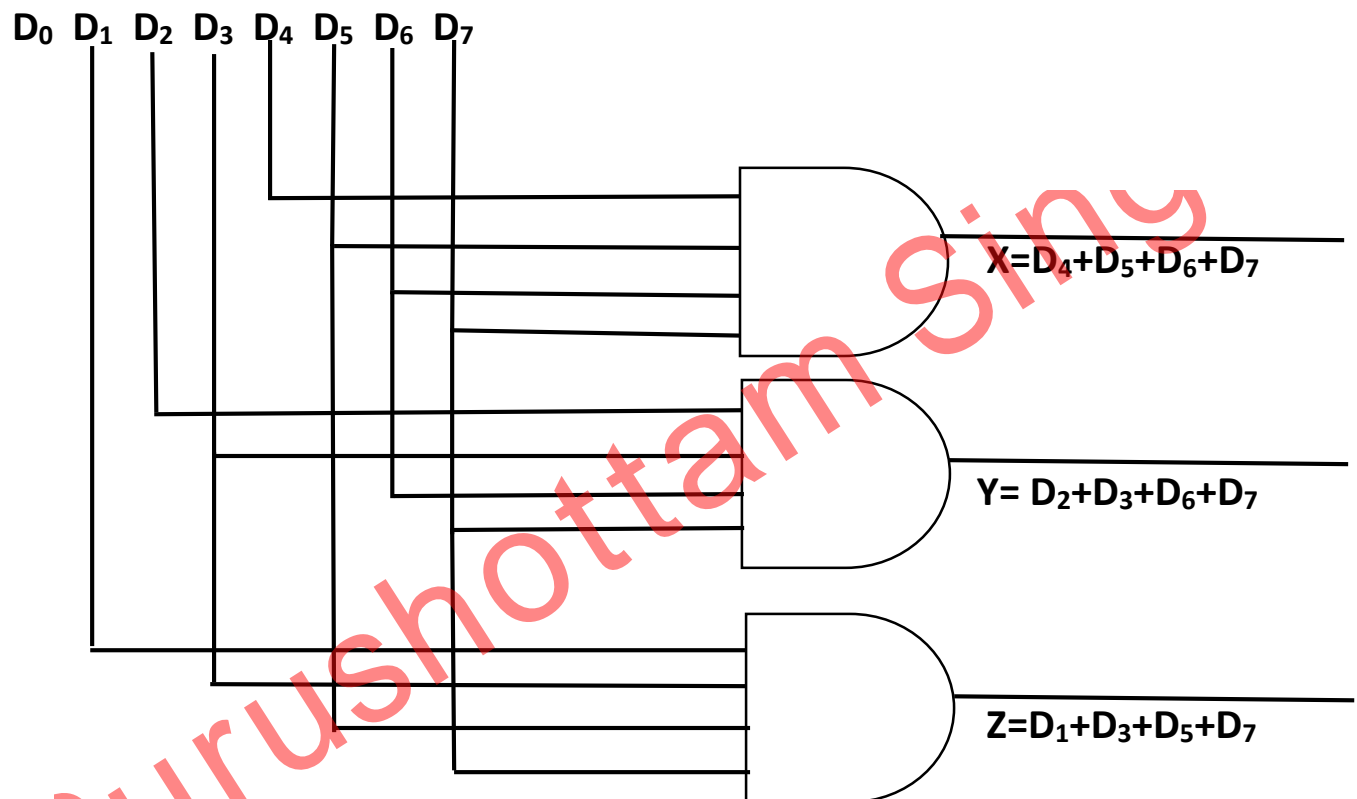

Q.8 write short note on 8 4 2 1 BCD code [BCD: - Binary Code Decimal].

Ans.

The 8 4 2 1 BCD code is a weighted code is also sequence is called so it is useful for mathematical operation.

In this code each decimal digits 0 to 9 is coded by 4 bit binary number.

It is called natural binary because of the 8 4 2 1 weight attached to it.

There are six invalid combinations 1010, 1011, 1100, 1101, 1110 & 1111 they are not a part of 8 4 2 1 BCD code.

Advantages of BCD code:-

- ~ It is easy to convert from decimal. Ex. 31 0011 0001

Disadvantages of BCD code:-

- ~ It required more bit to represent of number.

BCD Arithmetic:-

(1) Additions :-

BCD addition is performed by adding the corresponding digits of 4 bit binary.

If there is carry out a group to the next group or if the result is greater than 0110 (6) is called to the group.

(2) Subtraction:-

BCD subtraction is borrow from next row then 0110 (6) is subtracted from the group.

Q.9 Excess three code (XS-3)

Ans.

- ~ Excess-3 also called (XS-3) code.
- ~ Excess-3 also called non-weighted.

XS-3 code derived from each binary code corresponding 8 4 2 1 plus 0011 (3).

It can be used arithmetic operation.

Table of XS-3

Decimal	8	4	2	1	XS-3 code
0	0	0	0	0	0011 (0+3)=3
1	0	0	0	1	0100(1+3)=4
2	0	0	1	0	0101(2+3)=5
3	0	0	1	1	0110(3+3)=6
4	0	1	0	0	0111(4+3)=7
5	0	1	0	1	1000(5+3)=8
6	0	1	1	0	1001(6+3)=9
7	0	1	1	1	1010(7+3)=10
8	1	0	0	0	1011(8+3)=11
9	1	0	0	1	1100(8+4)=12

XS-3 code has six invalid state like 0000, 0001, 0010, 1101, 1110, 1111.